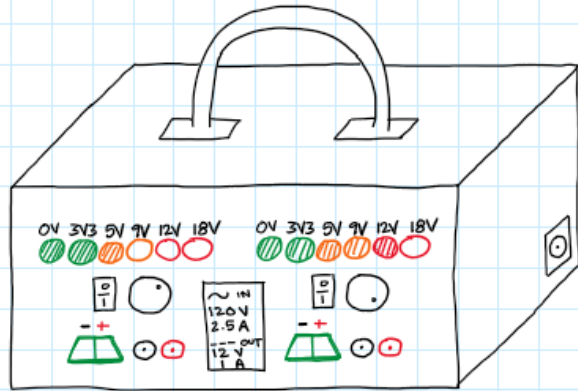


Design Requirements


Power Supply Requirements		Requirements language is to be interpreted as described in RFC 2119		
Hamza Dugmag	Revision 1.4	2022-09-07		
	Revision 1.3	2022-08-20		
	Revision 1.2	2022-08-15		
	Revision 1.0	2022-08-07		
	Revision 0.1	2022-07-16		

Requirement Number	Title	Description	Rationale, Comments	Verification Method
Functional Requirements				
SYS_F_001	Number of Channels	The design must have at least one channel	Primary functionality of a power supply	PCB review
SYS_F_002	Adjustable Channels	At least one channel must be voltage adjustable	Compatibility with a wide range of experiments and projects	PCB review
SYS_F_003	Constant Channels	There may be constant voltage channels	Ease of use when working with common voltages (e.g., 3.3V, 5V, 9V, 12V)	PCB review
SYS_F_004	Enclosure	The design must be enclosed in a 3D printed case	Permanent solution and aesthetics	CAD review
SYS_F_005	On/Off State	Each channel must be switched on and off individually using a rocker switch	Ease of use since there is no need to unplug/plug the AC-DC adapter each time	Experimental testing
SYS_F_006	LED Indicators	A row of LEDs per channel must indicate the on/off state and voltage level	Crude indicator to show the system is working properly; use a voltmeter for accurate reading	Experimental testing
SYS_F_007	LED Pattern	The LED voltage indicator colors and pattern may be arbitrary	E.g., green (> GND), green (>=3.3V), yellow (>=5V), yellow (>=9V), red (>=12V), red (>=18V)	CAD review
SYS_F_008	Number of Outputs	Each channel must have at least one output (any type of connection)	To power multiple circuits using the same voltage if desired	PCB review
SYS_F_009	Banana Plug Output	Each channel must contain banana plug outputs	To use alligator clips	PCB review
SYS_F_010	Voltage Adjust	All adjustable channels must be adjustable using physical interfaces	Ease of use; e.g. cylindrical knob	PCB review
SYS_F_011	Power Profile Sticker	The input and output voltage and current ranges must be indicated on the enclosure	Understandability, safety	CAD review
SYS_F_012	Financial Cost	The total cost of components must be less than C\$50	Cheaper than off-the-shelf solutions	BOM review
SYS_F_013	Anti-Slip	The design may not slip on wooden surfaces	Stability and safety	Experimental testing
SYS_F_014	Handle	The design may have a handle	Ease of use and portability	Experimental testing
SYS_F_015	Continuous Adjustment	Adjustable voltage channels must adjust the voltage continuously	Wider range of values	Experimental testing
SYS_F_016	LED Brightness	The LED indicators must be of similar brightness	Consistency and aesthetics	Inspection
SYS_F_017	Main Switch	The power supply may have a main rocker switch	Added layer of safety	PCB review
SYS_F_018	Heatsink	Voltage regulators may be cooled using heatsinks	Maintain efficiency and a safe temperature	BOM review
Performance Requirements				
SYS_P_001	Component Power Rating	All components must be rated to handle at least 1A 12V power supply output	Factor of safety	BOM review, PCB review
SYS_P_002	Inrush Current Limiting	Current may be limited as switches are turned on	Surge protection	PCB review
SYS_P_003	Voltage Stability	Input and output voltages must be stabilized using capacitors	Reduce noise	PCB review
SYS_P_004	Maximum Current Output	The design must output a maximum, limited current of at least 1A	Many projects may need 1A	BOM review
SYS_P_005	Fuse Rating	Fuses must be rated for about the maximum output current	Over-current protection	PCB review
SYS_P_006	Minimum Voltage Output	The design must output a minimum voltage of at most 3.3V	Many digital circuits can be powered at 3.3V	Experimental testing
SYS_P_007	Maximum Voltage Output	The design must output a maximum voltage of at least 12V	Many projects may need 12V	Experimental testing
SYS_P_008	Minimum Input Voltage	The input voltage must be at least the maximum output voltage	Voltage regulators will step down voltage	BOM review
SYS_P_009	Schmitt Trigger	All comparator circuits should have hysteresis	Mitigate noisy input	PCB review
SYS_P_010	Barrel Jack Shielding	The power barrel jack may be shielded	Improve performance and safety	BOM review
SYS_P_011	Diode Protection	All voltage regulators must be diode protected	Safety against reverse current and capacitor discharge	PCB review
SYS_P_012	Mounting Type	All components must be soldered onto through-hole perfboards	Permanent solution with secure attachment	PCB review
SYS_P_013	AC-DC Conversion	AC-DC conversion must occur within an AC-DC power adapter	Safety; avoid working with AC power	PCB review
SYS_P_014	Perfboard Isolation	All perfboards must be isolated from each other and the case	Safety and short prevention	CAD review
SYS_P_015	Perfboard Stability	All perfboards must be secured to the inside of the case using standoffs	Safety, short prevention, and durability	CAD review
SYS_P_016	RoHS Compliance	All components must be RoHS compliant	Health and environmental safety	BOM review

Sketches




IN: 100-110VAC 15A
OUT: 3V3-18V 1.5A

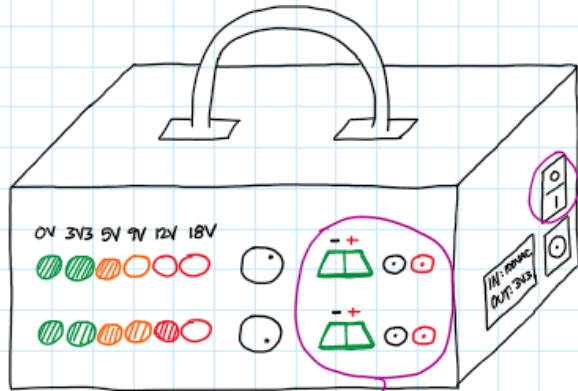

issue: turns on all channels

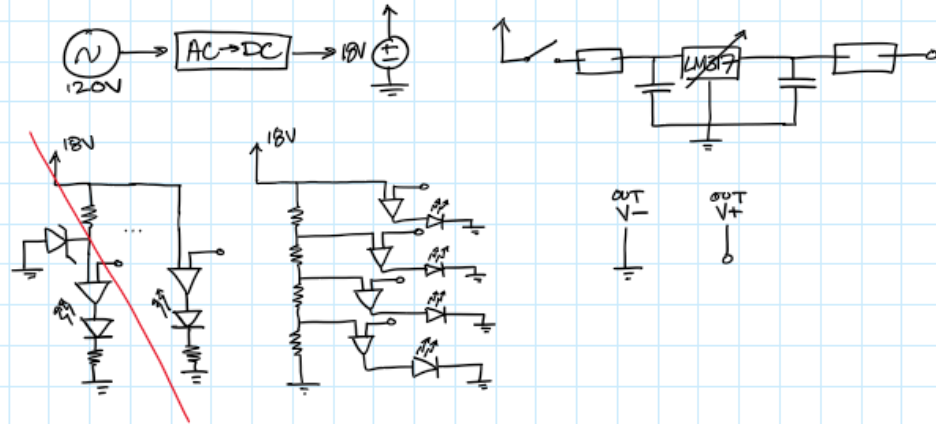issue: wires overlapping
→ ↓ safety
↓ ease of use



Circuit Calculations

```
1 def voltage_divider(vcc, resistances):
2     """
3     vcc: input voltage
4     resistances: array of series resistor values
5     return voltage at each node and current
6     """
7     assert len(resistances) > 0, "Short circuit!"
8
9     # macro-analysis
10    r_total = sum(resistances)
11    current = vcc/r_total
12
13    # array to return
14    voltages = [vcc]
15
16    v = vcc # voltage of current node
17    for r in resistances:
18        v -= r*current # count voltage drops
19        voltages.append(v)
20
21    voltages[-1] = 0 # fix floating point error
22
23    return voltages, current
24
25
26 def resistor_ladder(voltages, current):
27     """
28     voltages: node voltages along voltage divider
29     current: desired current
30     return series resistor values that satisfy voltages and current inputs
31     """
32    assert len(voltages) > 1, "Short circuit!"
33
34    # set ground to 0V
35    for i in range(len(voltages)):
36        voltages[i] -= voltages[-1]
37
38    # array to return
39    resistances = []
40
41    # observe equivalent resistance past current node
42    v = voltages[0]
43    r_total = v/current
```

```
37
38    # array to return
39    resistances = []
40
41    # observe equivalent resistance past current node
42    v = voltages[0]
43    r_total = v/current
44
45    for i in range(1, len(voltages)):
46        # split current equivalent resistance to two resistors
47        r = r_total - r_total*voltages[i]/v # r1 = r_total - r2
48        resistances.append(r)
49
50        # update current node voltage and equivalent resistance
51        v = voltages[i]
52        r_total = v/current
53
54    return resistances
55
56
57 def LED_resistor(vcc, vf, current):
58     vr = vcc - vf
59     r = vr/current
60     return r
61
62 def LED_current(vcc, vf, r):
63     vr = vcc - vf
64     current = vr/r
65     return current
66
67 if __name__ == "__main__":
68     # Voltage divider for LED circuit
69     print(resistor_ladder(voltages=[15.24, 12, 9, 5, 3.3, 0], current=0.001))
70     print(voltage_divider(15.24, [240, 3000, 3000, 4000, 1700, 3300]))
71
72     # LED circuit current draw
73     # LM339 maximum current is 20mA
74     # Brightness is approx. prop. to current
75     # print(LED_resistor(5, 1.8, 14/1000)) # red
76     # print(LED_resistor(5, 2.15, 14/1000)) # yellow
77     # print(LED_resistor(5, 2.95, 14/1000)) # green
```

Bill of Materials


Power Supply BOM		Adjustable single channel						
Hamza Dugmag	Revision 1.3	2022-09-07						
	Revision 1.2	2022-08-20						
	Revision 1.1	2022-08-15						
	Revision 1.0	2022-08-13						
#	Quantity	Supplier	Manufacturer Part Number	Description	Comments	Unit Price (CAD)	Extended Price (CAD)	
1	1	Digi-Key Canada	16-00224	AC/DC Wall Adapter 15V 36W	AC-DC Conversion	19.24	19.24	
2	1	Digi-Key Canada	54-00127	Shielded Barrel Jack 5.5x2.1mm	AC-DC Conversion	1.13	1.13	
3	3	Digi-Key Canada	ED2250/2	Terminal Block 2 Positions	Power Input	2.61	7.83	
4	1	Digi-Key Canada	MF72-005D9	Inrush Current Limiter 5R 3A	Both channels	0.55	0.55	
5	1	Digi-Key Canada	SW-R3-1A-A-1-0	SPST Subminiature Rocker Switch	Main and channel switches	0.265	0.265	
6	1	Digi-Key Canada	0697H0250-02	Fuse 250mA Slow Blow	5V linear regulator	0.51	0.51	
7	1	Digi-Key Canada	0697W1000-02	Fuse 1A Slow Blow	Adjustable linear regulators	0.4	0.4	
8	2	Digi-Key Canada	1N4934G-T	Diode 1A	Reverse current protection	0.434	0.868	
9	2	Digi-Key Canada	BAT46	Schottky Diode 150mA	Capacitor discharge protection	0.69	1.38	
10	1	Amazon Canada	Tn-19	Capacitor Ceramic 0.33u	5V linear regulator input	0.033	0.033	
11	3	Amazon Canada	Tn-19	Capacitor Ceramic 0.1u	Linear regulator and LM339 inputs	0.033	0.099	
12	1	Amazon Canada	Tn-19	Capacitor Ceramic 1u	CV linear regulator output	0.033	0.033	
13	1	Digi-Key Canada	BA17805CP-E2	IC Linear Voltage Regulator 5V 1A TO220	LEDs and LM339	1.86	1.86	
14	2	Digi-Key Canada	LM317BT	IC Linear Voltage Regulator Adjustable 1.5A TO220	Current limiter and voltage output	0.939	1.878	
15	2	Digi-Key Canada	507302B000000G	Heatsink TO220 2.5W	Adjustable linear regulators	0.328	0.656	
16	1	Digi-Key Canada	PTV09A-4225U-B103	Potentiometer 10k 1/20W Carbon Linear	Voltage adjustment	1.2	1.2	
17	1	Digi-Key Canada	COM-10001	Knob Knurled Metal	Potentiometer aesthetic	2.37	2.37	
18	6	Amazon Canada	An-resistor02	Resistor 1.8R 1% 1/4W	CC linear regulator output	0.0092	0.0552	
19	1	Amazon Canada	An-resistor02	Resistor 910R 1% 1/4W	CV linear regulator adjust	0.0092	0.0092	
20	1	Amazon Canada	An-resistor02	Resistor 240R 1% 1/4W	LM339 voltage divider	0.0092	0.0092	
21	2	Amazon Canada	An-resistor02	Resistor 3k 1% 1/4W	LM339 voltage divider	0.0092	0.0184	
22	1	Amazon Canada	An-resistor02	Resistor 3.9k 1% 1/4W	LM339 voltage divider	0.0092	0.0092	
23	1	Amazon Canada	An-resistor02	Resistor 100R 1% 1/4W	LM339 voltage divider	0.0092	0.0092	
24	1	Amazon Canada	An-resistor02	Resistor 1.5k 1% 1/4W	LM339 voltage divider	0.0092	0.0092	
25	1	Amazon Canada	An-resistor02	Resistor 200R 1% 1/4W	LM339 voltage divider	0.0092	0.0092	
26	1	Amazon Canada	An-resistor02	Resistor 3.3k 1% 1/4W	LM339 voltage divider	0.0092	0.0092	
27	5	Amazon Canada	An-resistor02	Resistor 1k 1% 1/4W	LED resistors	0.0092	0.046	
28	2	Amazon Canada	An-resistor02	Resistor 150k 1% 1/4W	LM339 Schmitt trigger (red LEDs)	0.0092	0.0184	
29	2	Amazon Canada	An-resistor02	Resistor 15k 1% 1/4W	LM339 Schmitt trigger (blue LEDs)	0.0092	0.0184	
30	1	Amazon Canada	LM339	IC Quad Differential Comparator	Voltage LED indicator	0.195	0.195	
31	1	Amazon Canada	S1121	14 Pin DIP Socket	LM339 socket	0.195	0.195	
32	1	Amazon Canada	n/a	White LED 5mm	Power Indicator	0	0	
33	2	Amazon Canada	n/a	Blue LED 5mm	Low Voltage Indicator	0	0	
34	2	Amazon Canada	n/a	Red LED 5mm	High Voltage Indicator	0	0	
35	1	Digi-Key Canada	PRT-09739	Banana Binding Post Red	Power output	0.63	0.63	
36	1	Digi-Key Canada	PRT-09740	Banana Binding Post Black	Ground output	0.63	0.63	
Total		58						42.17

Schematic Capture

Adjustable Power Supply


Single Channel 1.25–12V 0–1A

AC-DC Conversion

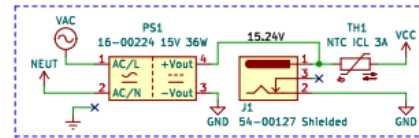


Power Supply

5V supply for LM339 and LEDs

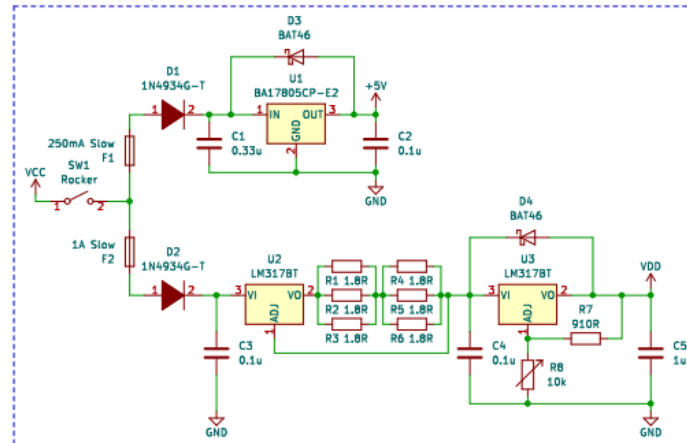


Voltage Indicator

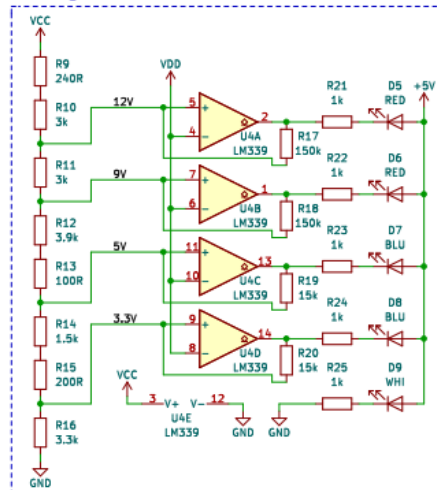

LED resistor values keep all LEDs at the same brightness (from inspection)
15(0)k resistors for hysteresis

Power Output

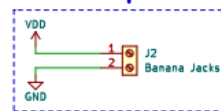

-1A maximum current
-0.2W maximum power across R1–R6
Regulate from 1.25V to -12V
Ceramic capacitors

Through-hole components

Hamza Dugmag

Sheet: /

File: PSU.kicad_sch

Title: Adjustable Power Supply



Size: USLetter Date: 2022-09-07

Rev: 1.6



KiCad E.D.A. eeschema (6.0.6)

Id: 1/1



LED Testing

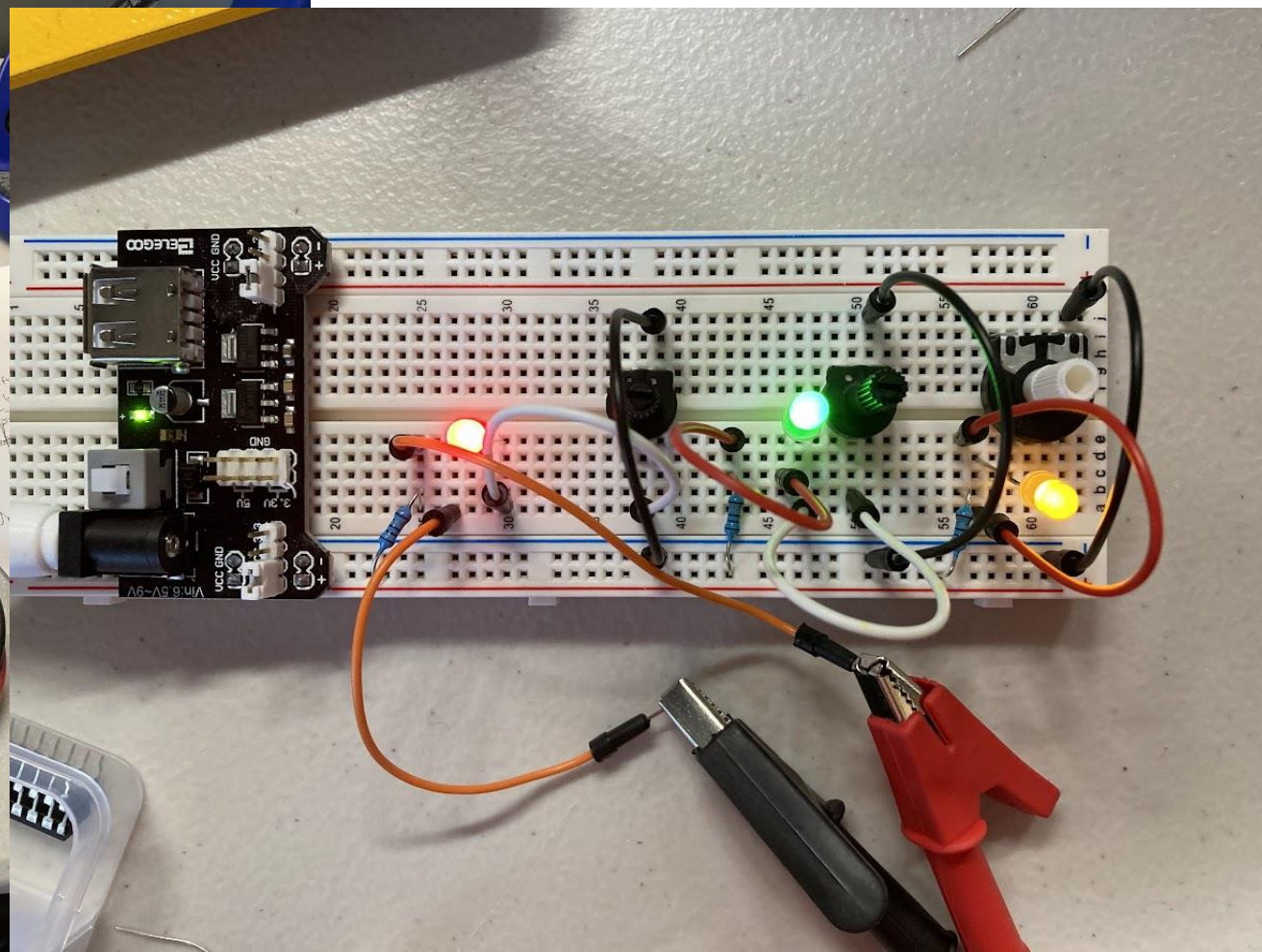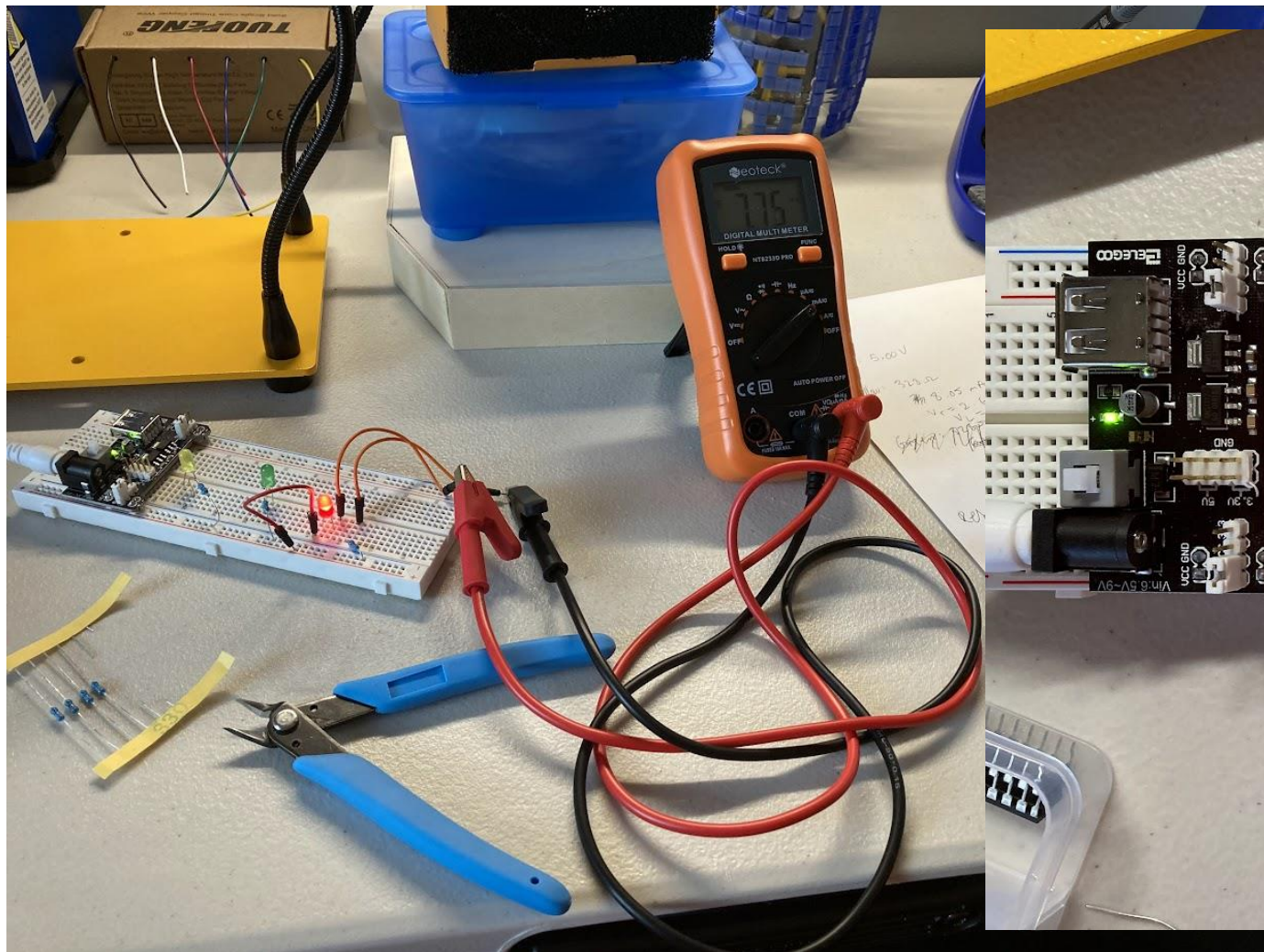

Power Supply: Breadboarding & Soldering

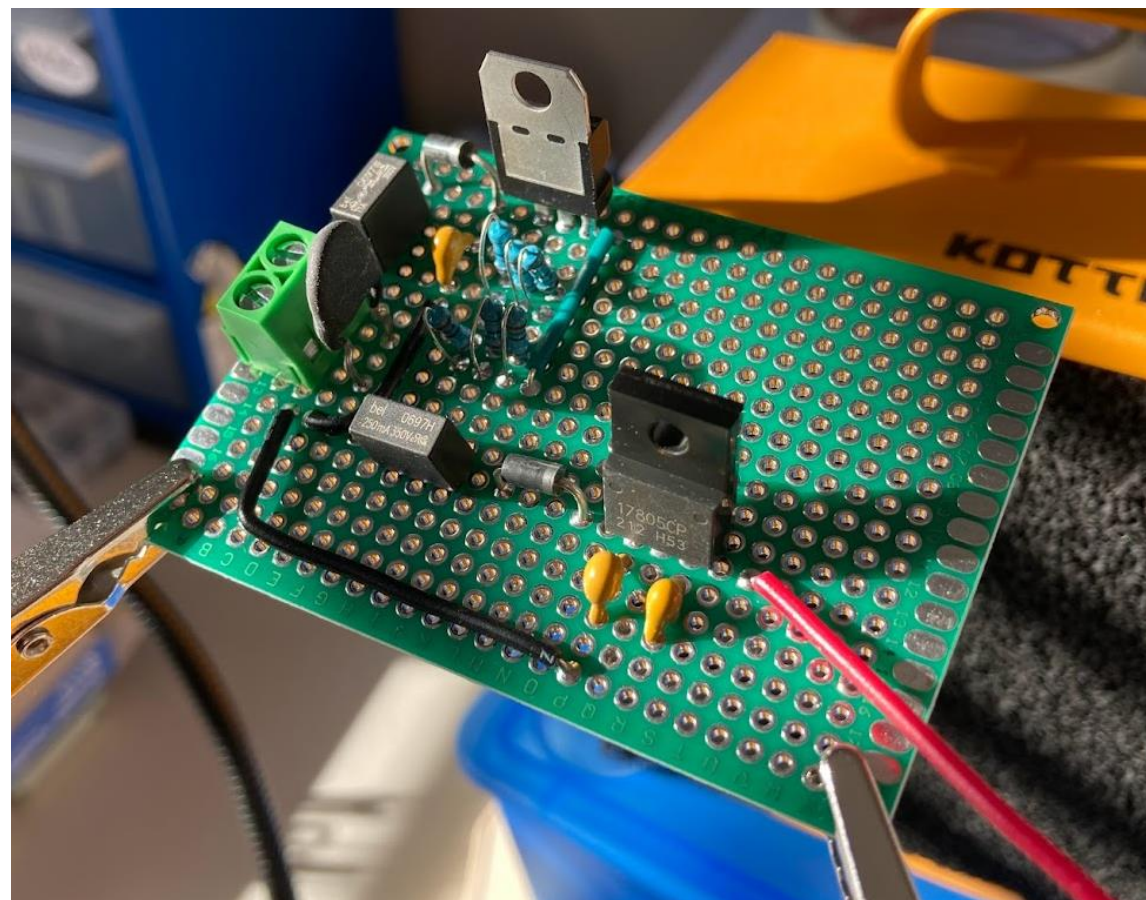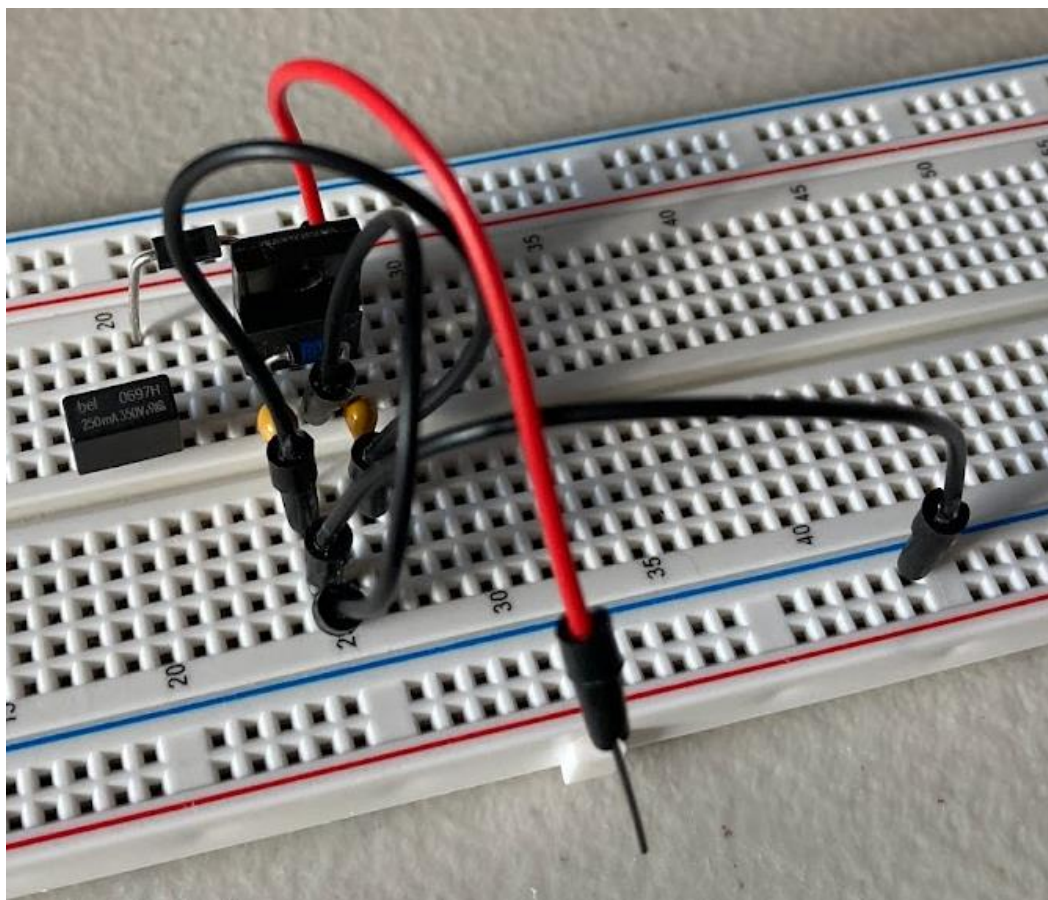

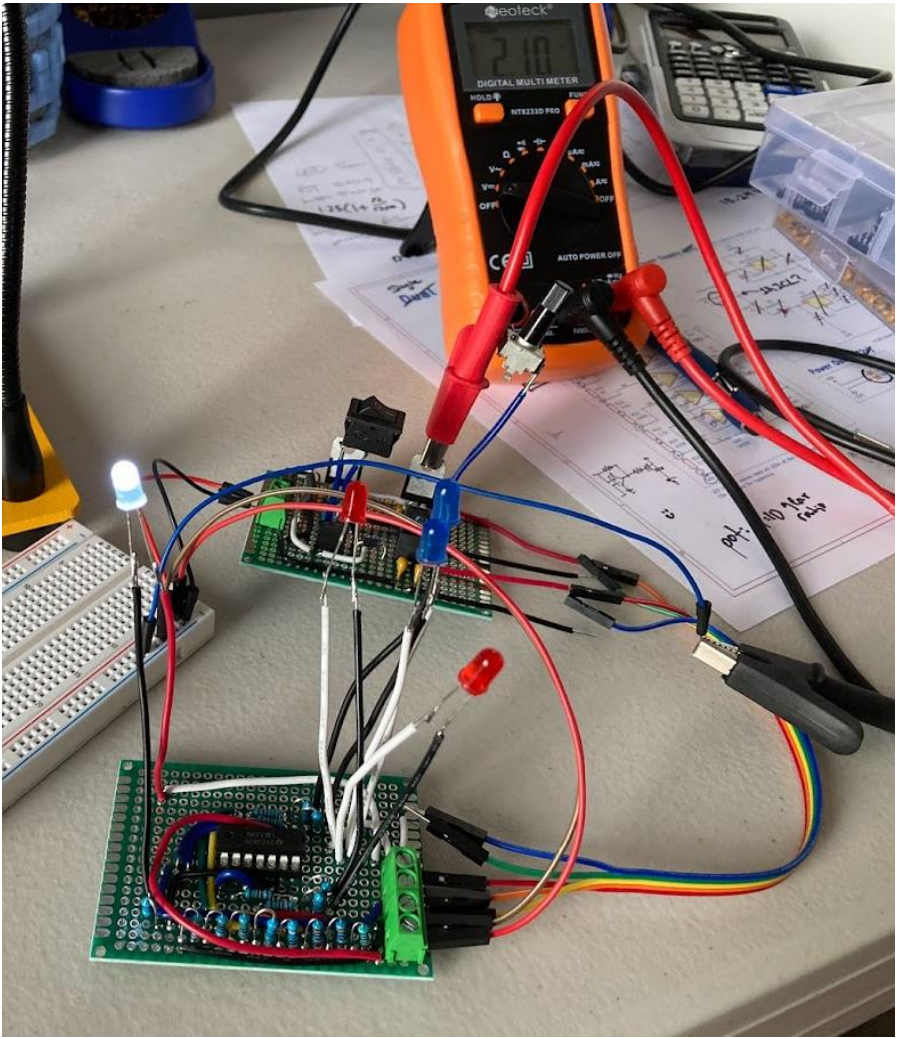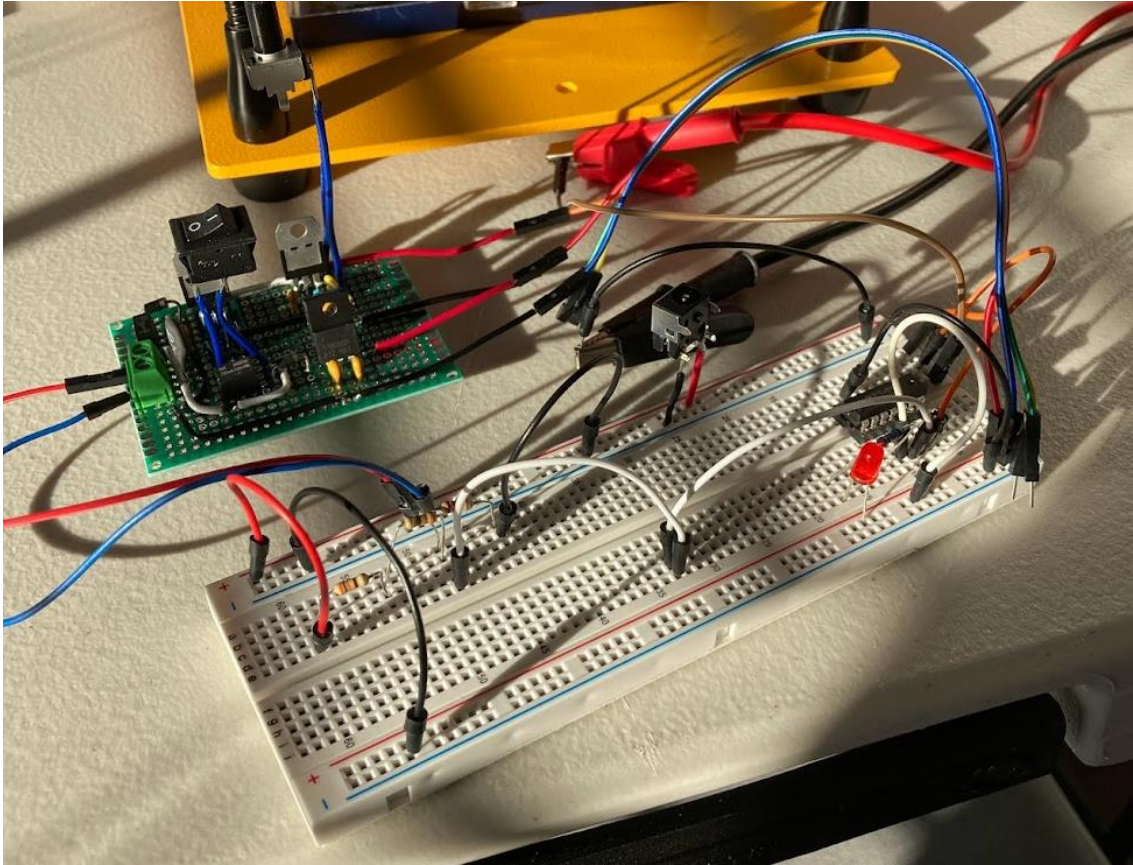Voltage Indicator: Breadboarding & Soldering



System Testing

